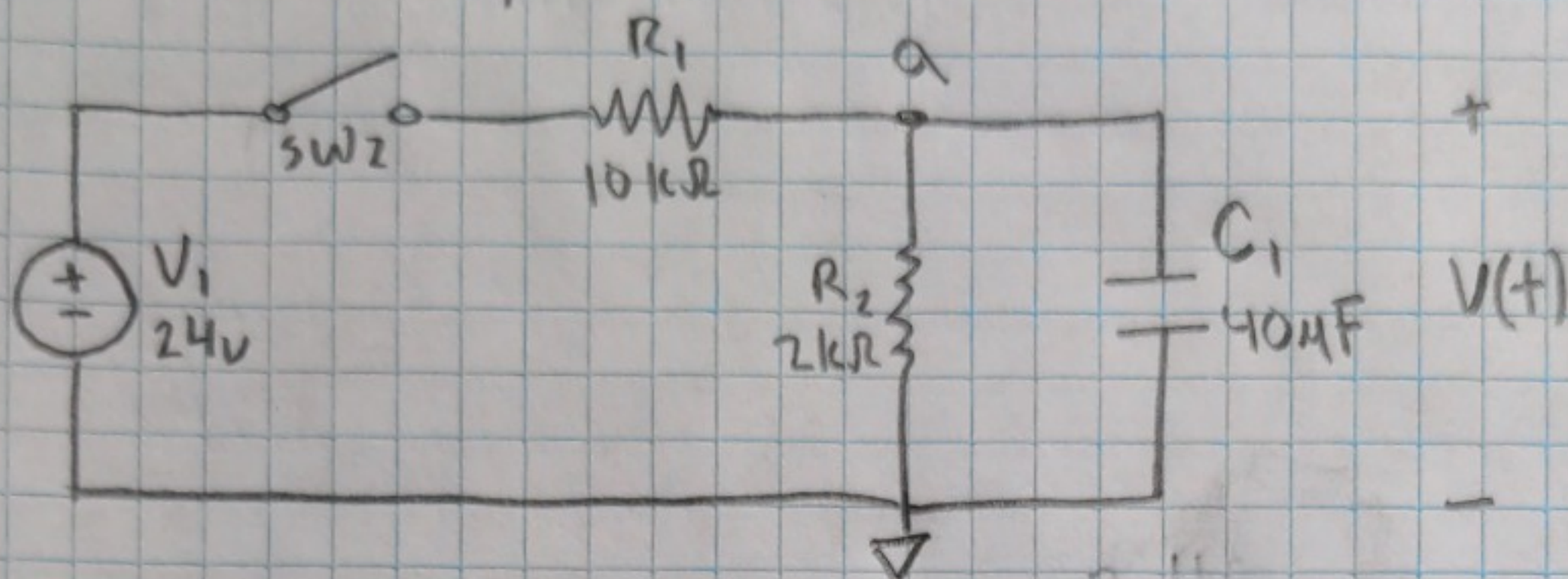



1.1) Find $v(t)$ for $t \geq 0$. SW2 has been closed for a long time and opens at $t=0$



V_a at $t \leq 0$) In a DC circuit, capacitors act as an open circuit.

$$V_a = V_1 \left(\frac{R_2}{R_1 + R_2} \right) = 24V \left(\frac{2k\Omega}{12k\Omega} \right) = \frac{24V}{6} = 4V$$

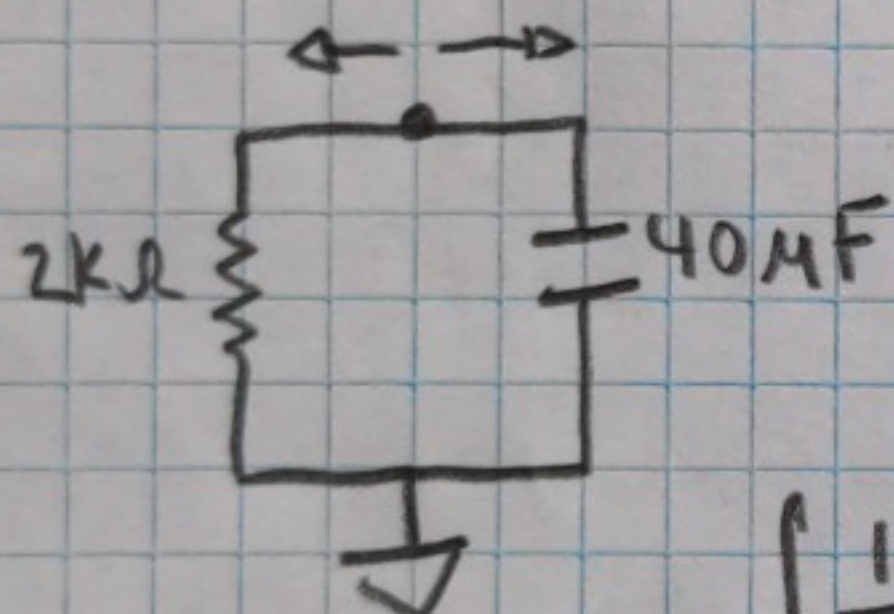At $t=0$ $V_c = V_a = 4V$, When SW2 opens effectively is:



$$R = 2k\Omega \quad C = 40\mu F \quad \tau = RC = .08$$

$$v(t) = V_c e^{-\frac{t}{\tau}} \rightarrow v(t) = 4 e^{-\frac{t}{.08}} V \text{ For } t \geq 0$$

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\frac{dv}{dt} + \frac{v}{RC} = 0$$

$$\frac{dv}{dt} = -\frac{v}{RC}$$

$$\frac{dv}{v} = -\frac{1}{RC} dt$$

$$\int \frac{1}{v} dv = -\frac{1}{RC} \int dt$$

$$\ln v + C_1 = -\frac{t}{RC} + C_2$$


$$\ln v = -\frac{t}{RC} + (C_2 - C_1); \quad C_2 - C_1 = \ln A$$

$$e^{\ln v} = e^{-\frac{t}{RC} + \ln A}$$

$$v(t) = A e^{-\frac{t}{RC}} \quad A = V_c \quad RC = \tau$$

$$v(t) = V_c e^{-\frac{t}{\tau}}$$

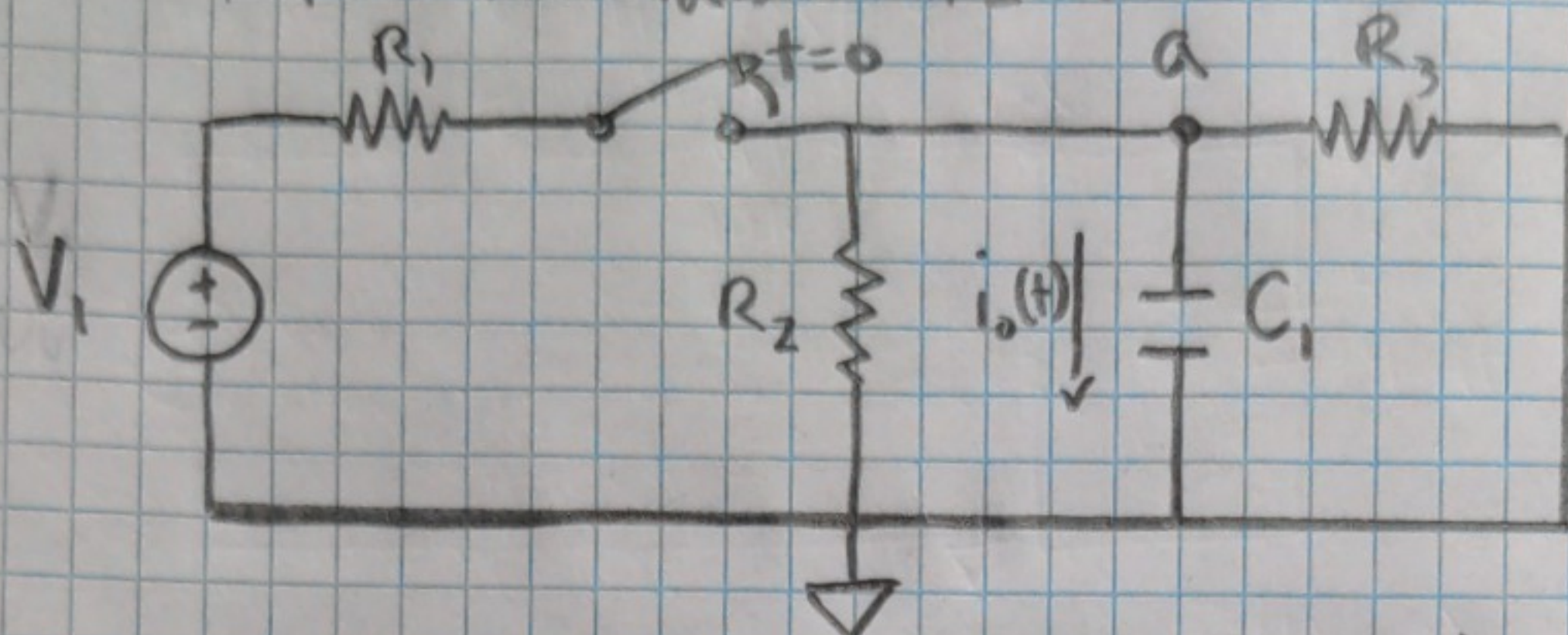1.2) The switch has been closed for a long time, and it opens at $t=0$. Find $i_o(t)$ for $t \geq 0$.



$$V_1 = 10\text{V}$$

$$R_1 = 4\text{k}\Omega$$

$$R_2 = 6\text{k}\Omega$$

$$R_3 = 12\text{k}\Omega$$

$$C_1 = 125\mu\text{F}$$

Find V_a at $t \leq 0$) $V_a = V_1 \left(\frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} \right)$

$$R_2 \parallel R_3 = \frac{(6\text{k}\Omega)(12\text{k}\Omega)}{18\text{k}\Omega} = 4\text{k}\Omega$$

$$V_a = 10\text{V} \left(\frac{4\text{k}\Omega}{8\text{k}\Omega} \right) = 5\text{V} = V_c$$


Find $V_c(t)$) $V_c(t) = V_c e^{-t/\tau}$

$$V_c(t) = 5e^{-2t}$$

$$R = R_2 \parallel R_3 = 4\text{k}\Omega \quad C = 125\mu\text{F}$$

$$\tau = RC = .5$$

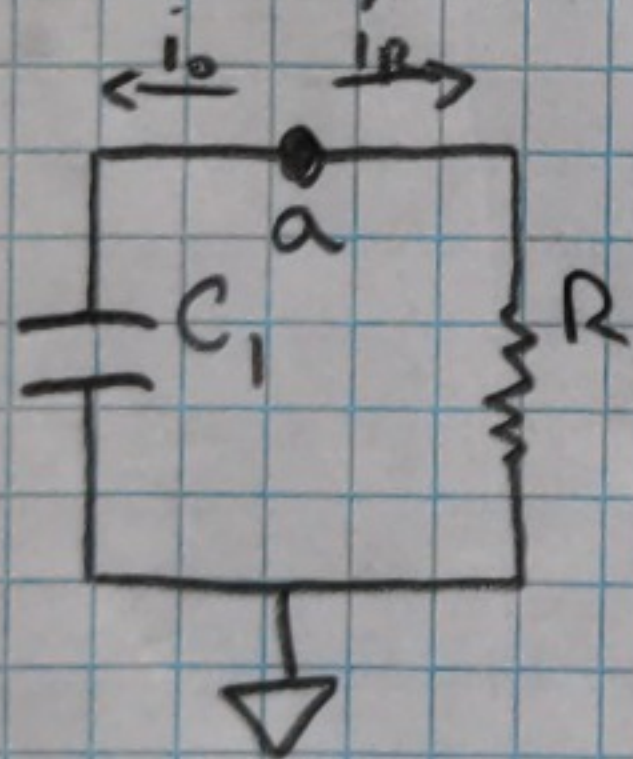Find $i_o(t)$) We can redraw the open switched circuit.




Using KCL, the current at (a) can be written as: $i_o + i_R = 0$

$$\text{So } \rightarrow i_o(t) = -i_R(t)$$

$$i_R(t) = \frac{V_c(t)}{R} \rightarrow \frac{5e^{-2t}\text{V}}{4\text{k}\Omega} = 1.25e^{-2t}\text{mA}$$

$$i_o(t) = -1.25e^{-2t}\text{mA}$$

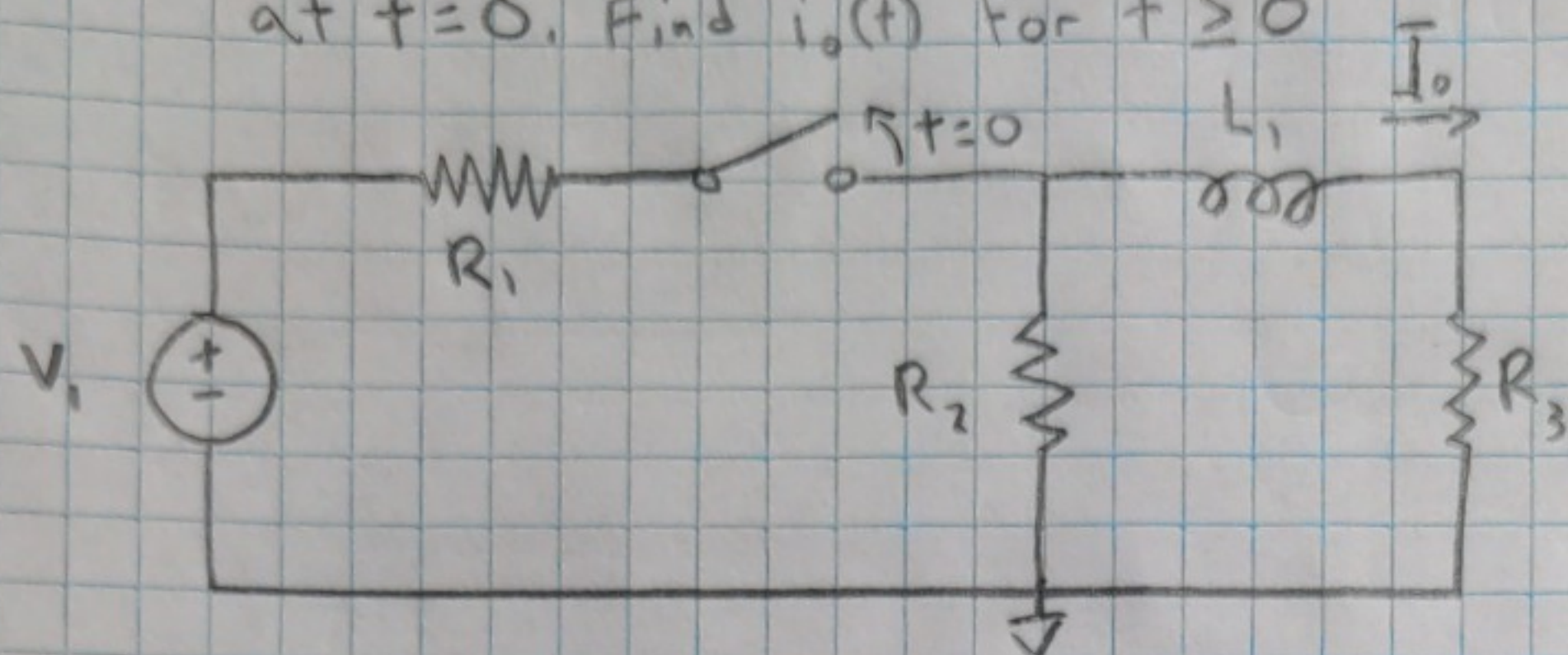1.3) The switch has been closed for a long time and opens at $t=0$. Find $i_o(t)$ for $t \geq 0$



$$V_1 = 24 \text{ V}$$

$$R_1 = 3 \Omega$$

$$R_2 = 4 \Omega$$

$$R_3 = 8 \Omega$$

$$L_1 = 4 \text{ H}$$

Find I_0 when $t < 0$ | L_1 acts as a short circuit.

$$I_0 = I_{\text{tot}} \left(\frac{R_2}{R_2 + R_3} \right)$$

$$I_{\text{tot}} = \frac{V_1}{R_{\text{tot}}}$$

$$R_{\text{tot}} = R_1 + R_2 \parallel R_3$$

$$I_0 = \frac{24}{17} \text{ A} \left(\frac{4 \Omega}{12 \Omega} \right)$$


$$I_{\text{tot}} = \frac{24 \text{ V}}{17/3 \Omega}$$

$$R_{\text{tot}} = 3 \Omega + \frac{8}{3} \Omega = \frac{17}{3} \Omega$$

$$I_0 = \frac{24}{17} \text{ A}$$

$$I_{\text{tot}} = \frac{72}{17} \text{ A}$$

Find $i_o(t)$ when $t \geq 0$ | $i_o(t) = I_0 e^{-t/\tau}$

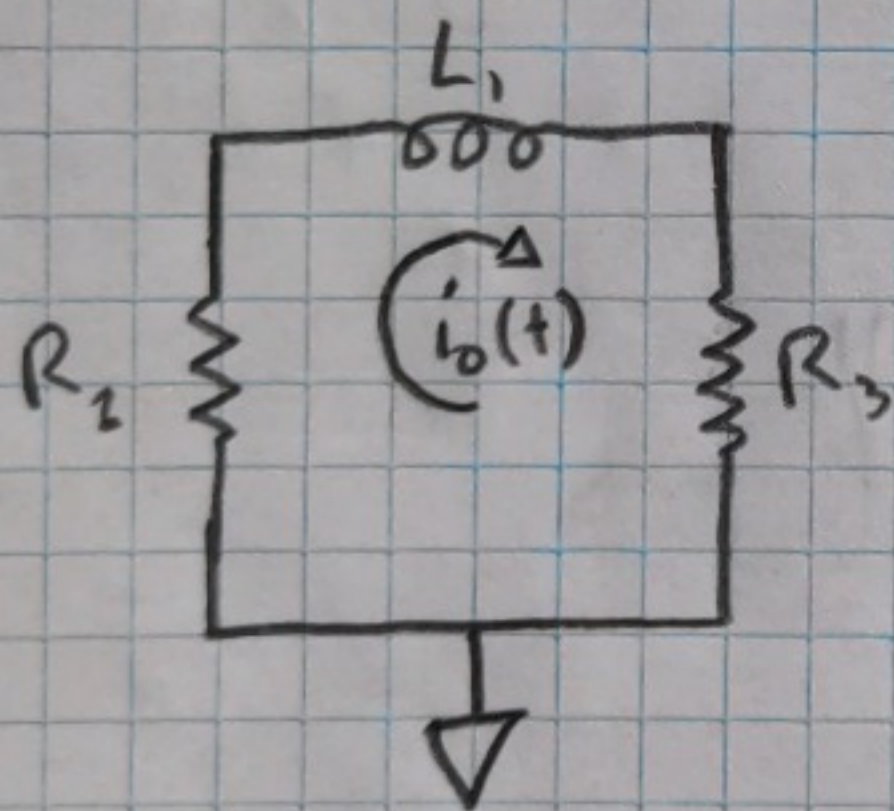


$$R = R_2 + R_3 = 12 \Omega$$

$$L_1 = 4 \text{ H}$$

$$\tau = \frac{L}{R} = \frac{4}{12} = \frac{1}{3}$$

$$i_o(t) = \frac{24}{17} e^{-3t} \text{ A}$$

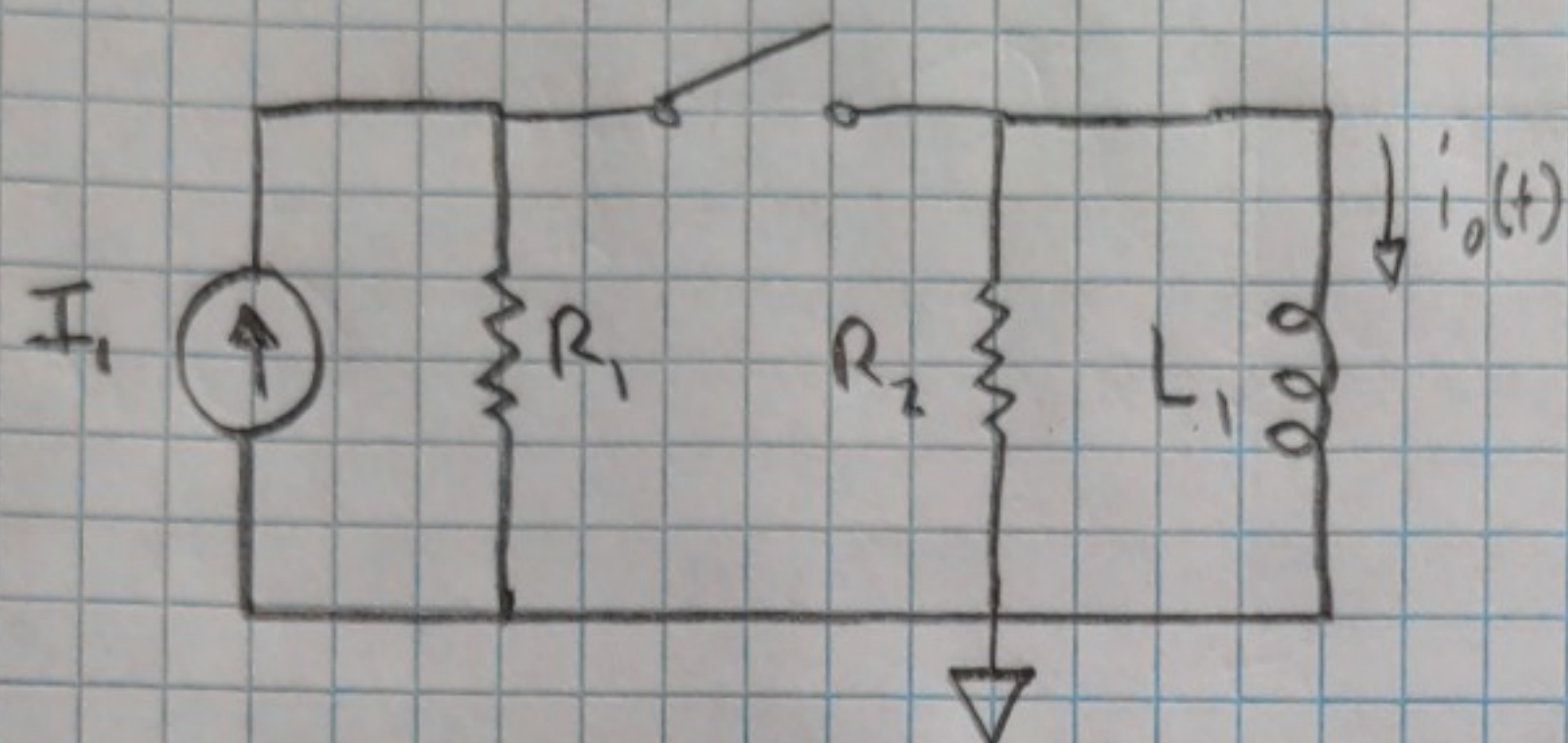1.4) Find the inductor current $i_o(t)$ for $t \geq 0$. The switch has been closed for $t < 0$ and opens at $t = 0$.



$$I_1 = 6 \text{ A}$$

$$R_1 = 4 \Omega$$

$$R_2 = 2 \Omega$$

$$L_1 = 3 \text{ H}$$

At $t < 0$, the inductor acts as a short circuit, therefore the current when $t < 0$ through L_1 is 6 A

$$I_0 = 6 \text{ A}$$

Find $i_o(t)$ $i_o(t) = I_0 e^{-t/\tau}$

$$\tau = \frac{L}{R} = \frac{3 \text{ H}}{2 \Omega}$$

$$i_o(t) = 6 e^{-\frac{2}{3}t} \text{ A}$$