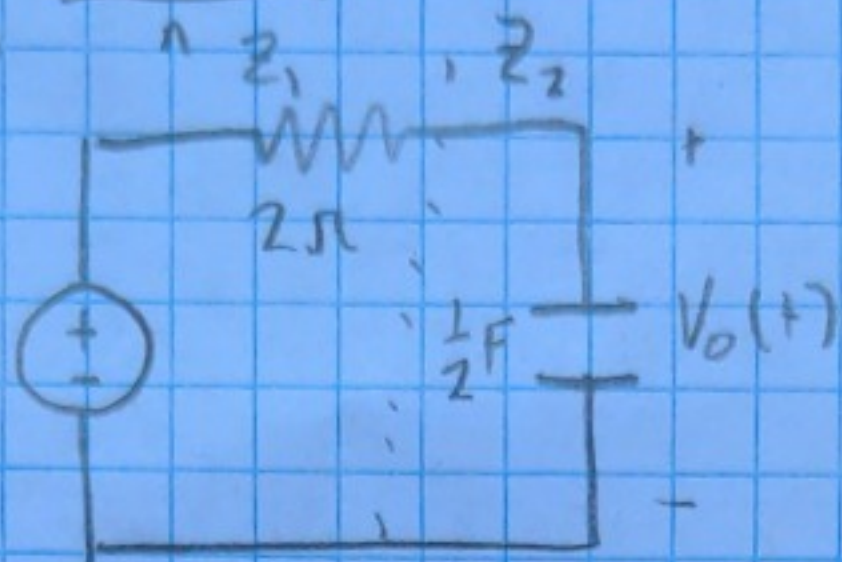


15.1) The voltage source $v_s(t)$ in the circuit is described by the Fourier Series.

$$v_s(t) = \frac{A}{2} - \frac{A}{\pi} \sum_{k=1}^{\infty} \frac{\sin(n\omega_0 t)}{n} \quad A = 5V \quad \omega_0 = \pi \frac{\text{rad}}{s} \rightarrow \omega_n = n\pi \frac{\text{rad}}{s}$$

$$k = 2n - 1$$



$$C = \frac{1}{2}F \quad Z_2 = \frac{2}{j\pi n}$$

$$\frac{Z_2}{Z_1 + Z_2} = \frac{\frac{2}{j\pi n}}{2 + \frac{2}{j\pi n}} = \frac{2}{2 + j2\pi n} = \frac{1}{1 + j\pi n}$$

Find $v_o(t)$ Begin by finding the DC component.

Since at DC the capacitor acts like an open circuit, $v_{o,DC}$ is equal to the DC component to our excitation voltage v_s .

$$v_{o,DC} = \frac{5}{2}V$$

Let's rewrite the ac component in phasor form.

$$v_s = \frac{5}{\pi n} \sin(n\omega_0 t) = \frac{5}{\pi n} \cos(n\omega_0 t + 90^\circ) \quad \omega_n = n\omega_0$$

$$v_s = \frac{5}{\pi} \angle 90^\circ V$$

Now rewrite $\frac{Z_2}{Z_1 + Z_2}$ in phasor form:

$$\frac{Z_2}{Z_1 + Z_2} = \frac{1}{1 + j\pi n} = \frac{1 \angle 0}{\sqrt{1 + (\pi n)^2} \angle \tan^{-1} \pi n}$$


Find v_o using a voltage divider

$$v_o = \frac{\frac{5}{\pi n} \angle 90^\circ}{\sqrt{1 + (\pi n)^2} \angle \tan^{-1} \pi n}$$

$$v_o = \frac{5}{\pi n \sqrt{1 + \pi^2 n^2}} \angle 90^\circ - \tan^{-1} \pi n$$

$$v_o(t) = \frac{5}{2} + \sum_{n=1}^{\infty} \frac{5}{n\pi \sqrt{1 + \pi^2 n^2}} \cos(n\pi t + 90^\circ - \tan^{-1} \pi n) V$$

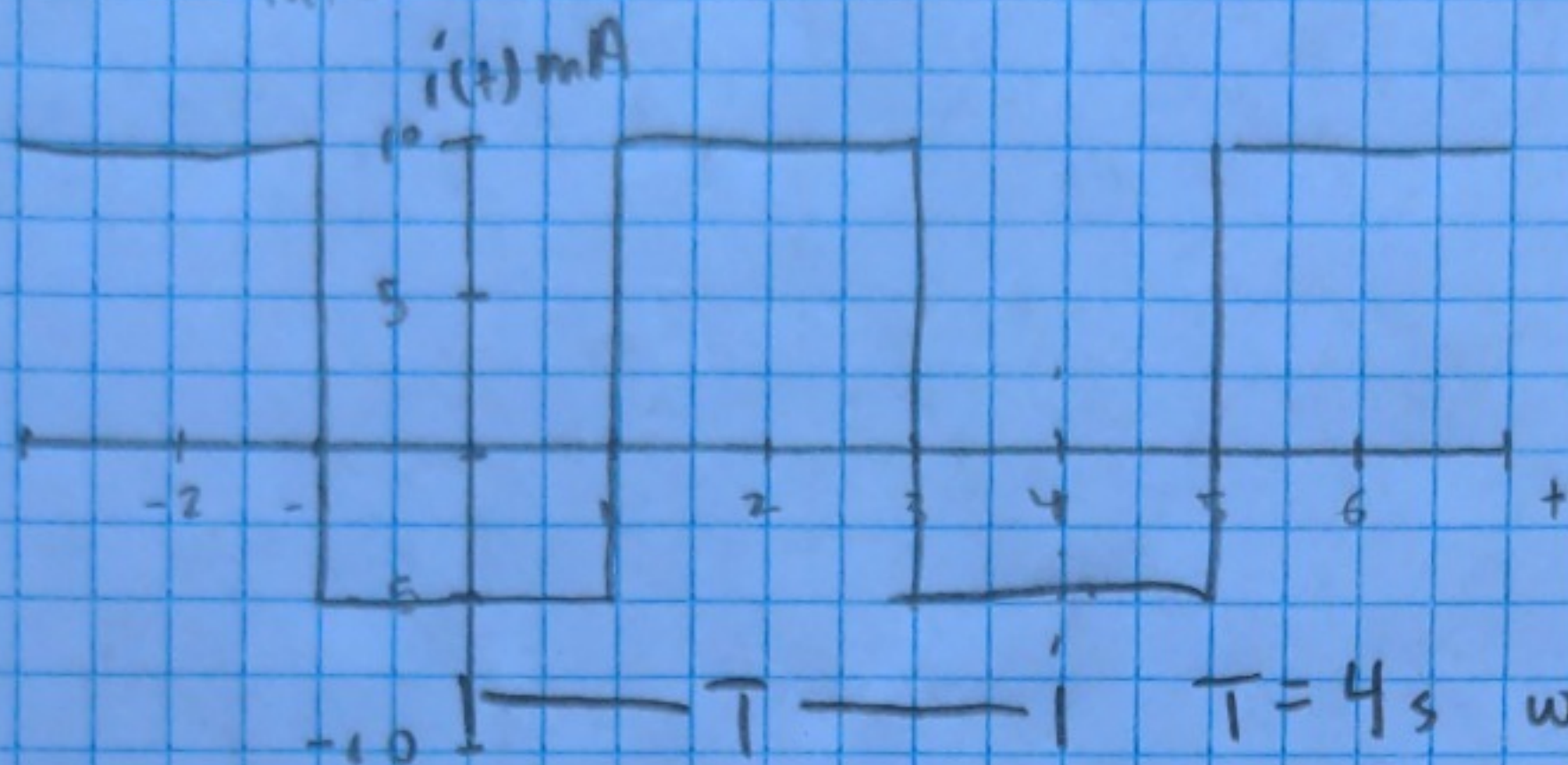15.2) The following waveform describes the current being fed into a $1.5k\Omega$ resistor.



Even symmetry!

$$a_0 = \frac{2}{T} \int_0^{T/2} F(t) dt$$

$$a_n = \frac{4}{T} \int_0^{T/2} F(t) \cos(n\omega_0 t) dt$$

$$b_n = 0$$

a) Find the power dissipated in the resistor using Fourier Series

$$a_0 = \frac{2}{4} \left(\int_0^1 -5 dt + \int_1^2 10 dt \right)$$

$$a_0 = \frac{1}{2} (-5 + 10)$$

$$a_0 = \frac{5}{2} \text{ mA}$$

$$a_n = \frac{4}{4} \left(\int_0^1 -5 \cos(n\omega_0 t) dt + \int_1^2 10 \cos(n\omega_0 t) dt \right)$$

$$a_n = \frac{-5 \cdot 2}{\pi n} \left(\sin(n\frac{\pi}{2}t) \Big|_0^1 \right) + \frac{10 \cdot 2}{\pi n} \left(\sin(n\frac{\pi}{2}t) \Big|_1^2 \right)$$

$$a_n = -\frac{10}{\pi n} \sin(n\frac{\pi}{2}) + \frac{20}{\pi n} \left(\sin(n\pi) - \sin(n\frac{\pi}{2}) \right)$$

$$a_n = -\frac{30}{\pi n} \sin(n\frac{\pi}{2}) \Rightarrow i(t) = \frac{5}{2} - \frac{30}{\pi} \sum_{k=1}^{\infty} \frac{(-1)^{k-1}}{n} \cos(\frac{\pi}{2}nt) \text{ mA}$$

$$n = 2k-1$$

$$P_{1\Omega} = I_{rms}^2 = a_0^2 + \frac{1}{2} \sum_{k=1}^{\infty} a_n^2 + b_n^2$$

$$P_{1\Omega} = \frac{25}{4} + \frac{1}{2} \left(\left(\frac{-30}{\pi} \right)^2 + \left(\frac{10}{\pi} \right)^2 + \left(\frac{-6}{\pi} \right)^2 \right)$$

$$P_n = \frac{25}{4} + \frac{518}{\pi^2} = 58.73 \text{ mW}$$

$$1000\Omega \cdot P_n = 58.73 \text{ W}$$

Chris Hunt

HW15

ENGR 203

15.2) b) What fractions of the total power dissipated in the resistor are due to the DC component and 1st harmonic?

$$P_{in} = \frac{25}{4} + \frac{1}{2} \left(\frac{400}{\pi^2} \right) = 51.84 \text{ mW}$$

$$1000 \text{ k}\Omega \cdot P_{in} = 51.84 \text{ W}$$

$$\frac{51.84 \text{ W}}{58.73 \text{ W}} \cdot 100 = 88.27\%$$

The DC and 1st Harmonic comprise 88.27% of the power dissipated through the resistor.