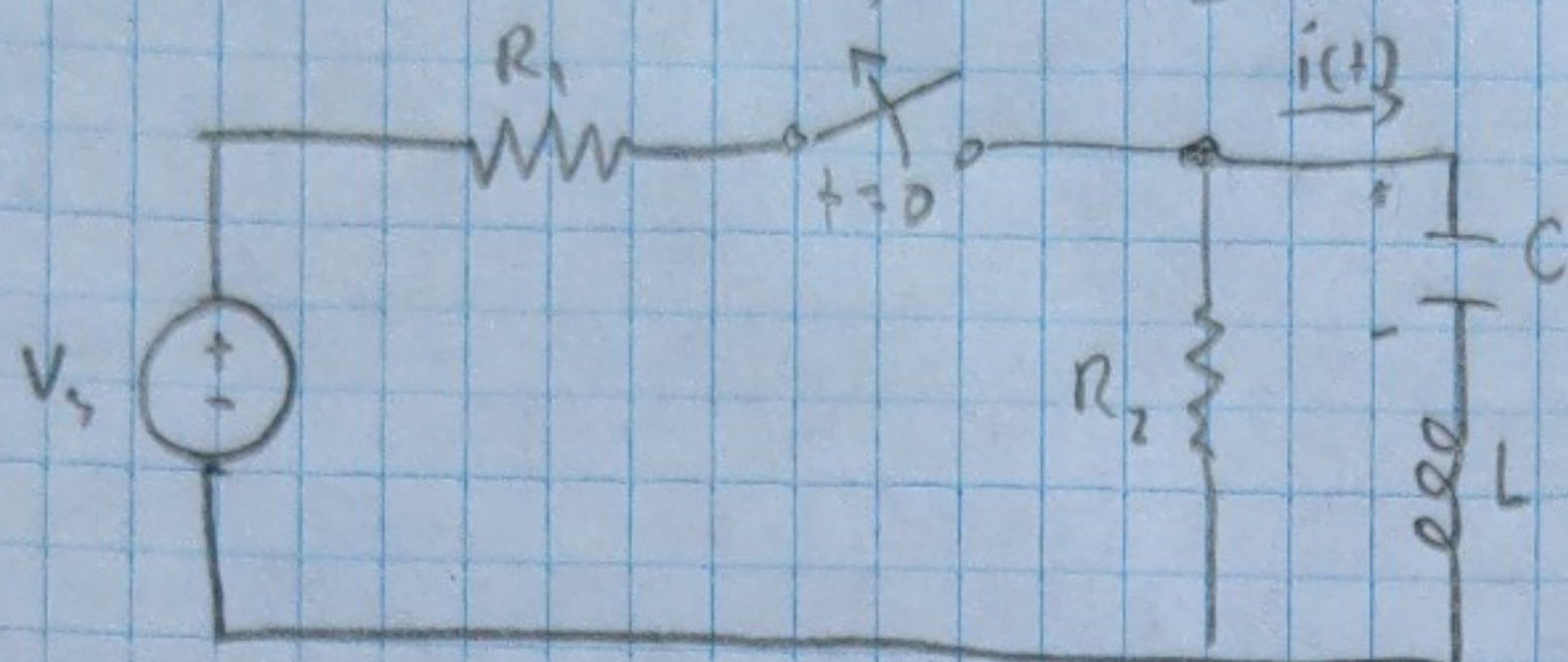


5.1) The switch has been closed for a very long time and opens at $t=0$. Find $i(t)$ for $t \geq 0$.



$$V_s = 20V$$

$$R_1 = 10\Omega$$

$$R_2 = 40\Omega$$

$$C = 1\text{mF}$$

$$L = 2.5H$$


t	i_L	V_C	$\frac{di_L}{dt}$	$\frac{dV_C}{dt}$
0^-	0A	16V	0A/s	0V/s
0^+	0A	16V	-6.4 A/s	0V/s
∞	0A	0V	0A/s	0V/s

$$t = 0^-) \quad i_L = 0A$$

$$V_C = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

$$V_C = 16V$$

$t = 0^+)$

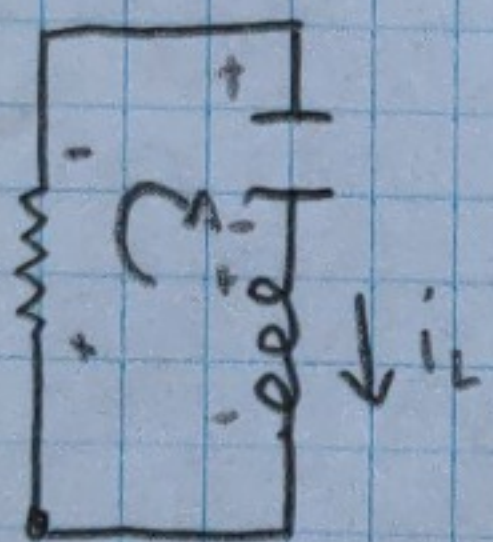

Find $\frac{di_L}{dt}$ $\frac{di_L}{dt} = \frac{V_L}{L}$

KVL) $+V_{R_1} + V_C + V_L = 0$

$$0 + 16V + V_L = 0 \rightarrow V_L = -16V$$

$$\frac{di_L}{dt} = \frac{-16V}{2.5H} = -6.4 A/s$$

$$\frac{dV_C}{dt} = \frac{i_C}{C} \rightarrow \frac{0}{C} = 0 V/s$$

Find $i(t)$ for $t \geq 0$

$$R = 40\Omega \quad C = 1\text{mF} \quad L = 2.5H$$

$$\alpha = \frac{R}{2L} = \frac{40\Omega}{5H} = 8 \text{ NP/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 20 \text{ rad/s} \rightarrow \alpha < \omega_0$$

under damped complex roots

Find ω_d $\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{336} \text{ rad/s}$

$$i(t) = e^{-8t} (B_1 \cos(\sqrt{336}t) + B_2 \sin(\sqrt{336}t)) A$$

$$\frac{di(t)}{dt} = -8e^{-8t} (B_1 \cos(\sqrt{336}t) + B_2 \sin(\sqrt{336}t)) + e^{-8t} (-\sqrt{336} B_1 \sin(\sqrt{336}t) + \sqrt{336} B_2 \cos(\sqrt{336}t))$$

cont.

Chris Hunt

HW 5

ENGR203

5.1) cont.


$$i(0) = 0 \text{ A} = B_1$$

$$\frac{di(0)}{dt} = -6.4 \text{ A/s} = -8 B_1 + \sqrt{336} B_2$$


$$\frac{di(0)}{dt} = -6.4 \text{ A/s} = \sqrt{336} B_2$$

$$B_2 = -\frac{6.4}{\sqrt{336}} \approx -0.349$$
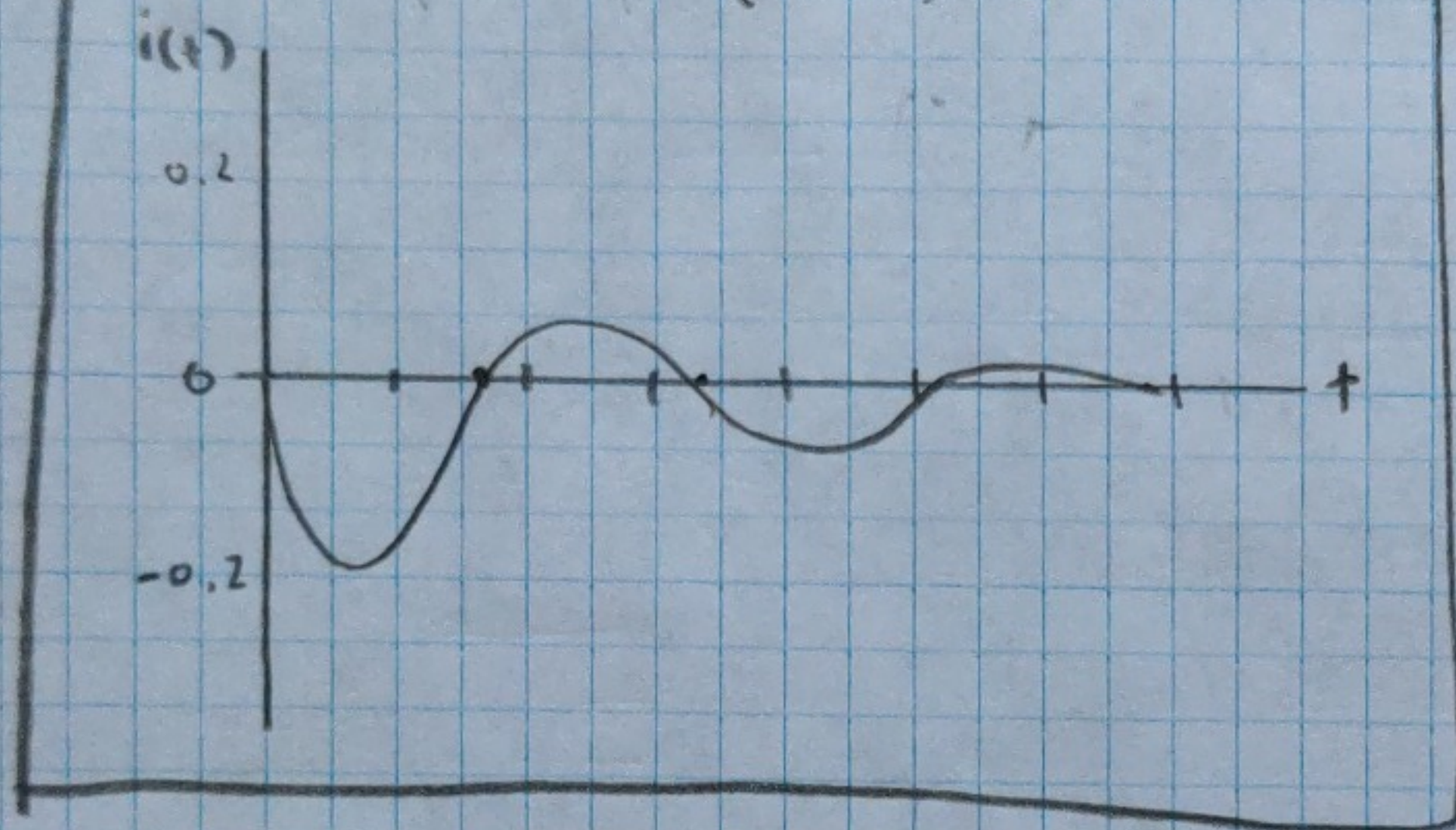
$$i(t) = -0.349 e^{-8t} \sin(\sqrt{336} t) \text{ A}$$



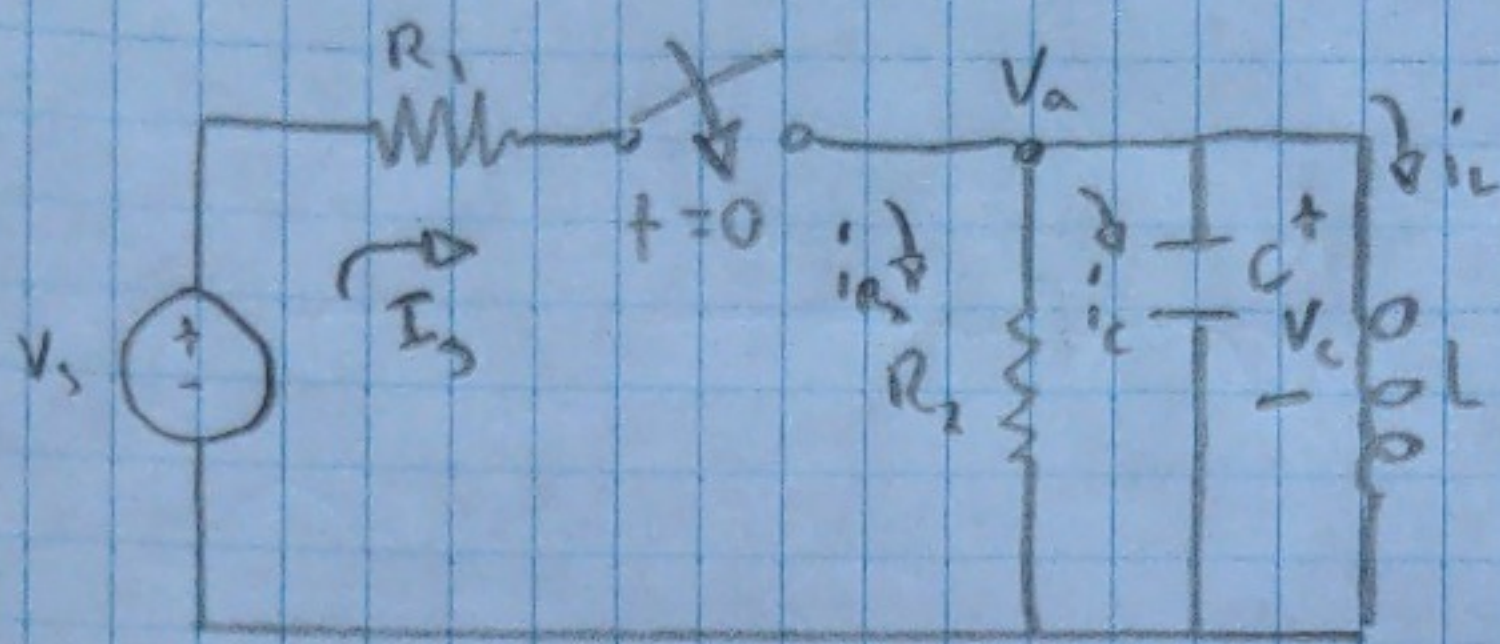5.2) Find $V_c(t)$ for $t > 0$. Assume initial conditions are 0.



$$V_s = 20V \quad R_1 = 5\Omega \quad R_2 = 1\Omega$$

$$C = 1F \quad L = 250mH$$

$$V_c(0^-) = 0V \quad i_C(0^-) = 0A$$

$$i_L(0^-) = 0A$$

t	i_L	V_c	$\frac{di_L}{dt}$	$\frac{dV_c}{dt}$
0^-	$0A$	$0V$	0A/s	0V/s
0^+	$0A$	$0V$	$0A/s$	$4V/s$
∞	$0A$	$0V$	0A/s	0V/s

At $t=0^+$ Since the capacitor maintains the voltage at V_a at $0V$, the voltage across L is $0V$.

$$V_L = 0V \rightarrow \frac{di_L}{dt} = \frac{V_L}{L} = \frac{0V}{250mH} = 0A/s$$

Find dV_c/dt $\frac{dV_c}{dt} = \frac{i_C}{C}$

Kcl @ a) $I_s = i_R + i_C + i_L \rightarrow \frac{20V}{5\Omega} = \frac{0V}{1\Omega} + i_C + 0A$

$$4A = i_C \rightarrow \frac{dV_c}{dt} = \frac{4A}{1F} = 4V/s$$

Find $V_c(t)$ $V_c(t) = V_f + V_{ss}$

$$V_{ss} = V_c(\infty) = 0V$$

$$I_s = \frac{20V}{5\Omega} = 4A$$

$$R_T = \frac{5}{6}\Omega$$

$$C = 1F$$

$$L = 250mH$$

$$\alpha = \frac{1}{2RC} = \frac{1}{10/6} = \frac{3}{5} \text{ NP/s}$$


$$\omega_0 = \frac{1}{\sqrt{L/C}} = 2 \text{ rad/s}$$

$\alpha < \omega_0 \rightarrow$ under damped

$$\omega_d = \sqrt{2^2 - (3/5)^2} = 3.64 \text{ rad/s}$$

$$V(t) = e^{-3/5t} (B_1 \cos(3.64t) + B_2 \sin(3.64t))$$
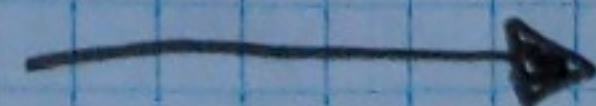
$$\frac{dV(t)}{dt} = -\frac{3}{5} e^{-3/5t} (B_1 \cos(3.64t) + B_2 \sin(3.64t)) + e^{-3/5t} (-3.64 B_1 \sin(3.64t) + 3.64 B_2 \cos(3.64t))$$



Chris Hunt

HW5

ENGR 203

5.2) Cont.


$$V(0) = 0 \text{ V} = e^0 (B_1 \cos(0) + B_2 \sin(0)) = B_1 = 0$$

$$\frac{dV(0)}{dt} = -\frac{3}{5} e^0 (B_1 \cos(0) + B_2 \sin(0)) + e^0 (-3.64 B_1 \sin(0) + 3.64 B_2 \cos(0))$$

$$\frac{dV(0)}{dt} = 4 \text{ V/s} = 3.64 B_2 \Rightarrow B_2 = 1.1 \text{ A}$$


$$V(t) = e^{-3/5 t} (1.1 \sin(3.64 t)) \text{ V}$$

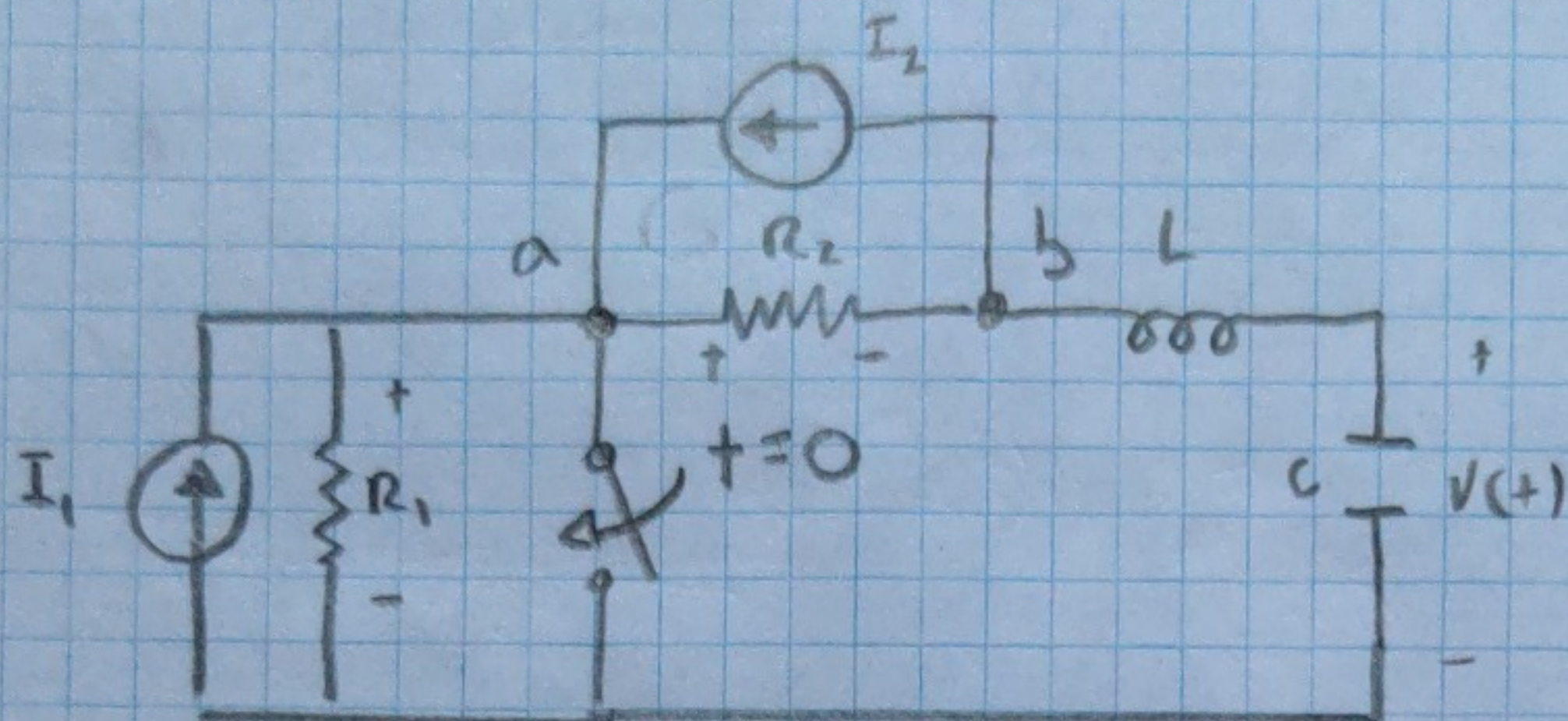5.3) Find $v(t)$ for $t > 0$. The switch has been open for a long time and closes at $t = 0$.



$$I_1 = 4A \quad I_2 = 2A \quad R_1 = 1\Omega \quad R_2 = 6\Omega \quad L = 1H \quad C = 40mF$$

t	i_L	V_C	$\frac{di_L}{dt}$	$\frac{dV_C}{dt}$
0^-	0A	-8V	0A/s	0V/s
0^+	0A	-8V		0V/s
∞	0A	0	0A/s	0V/s

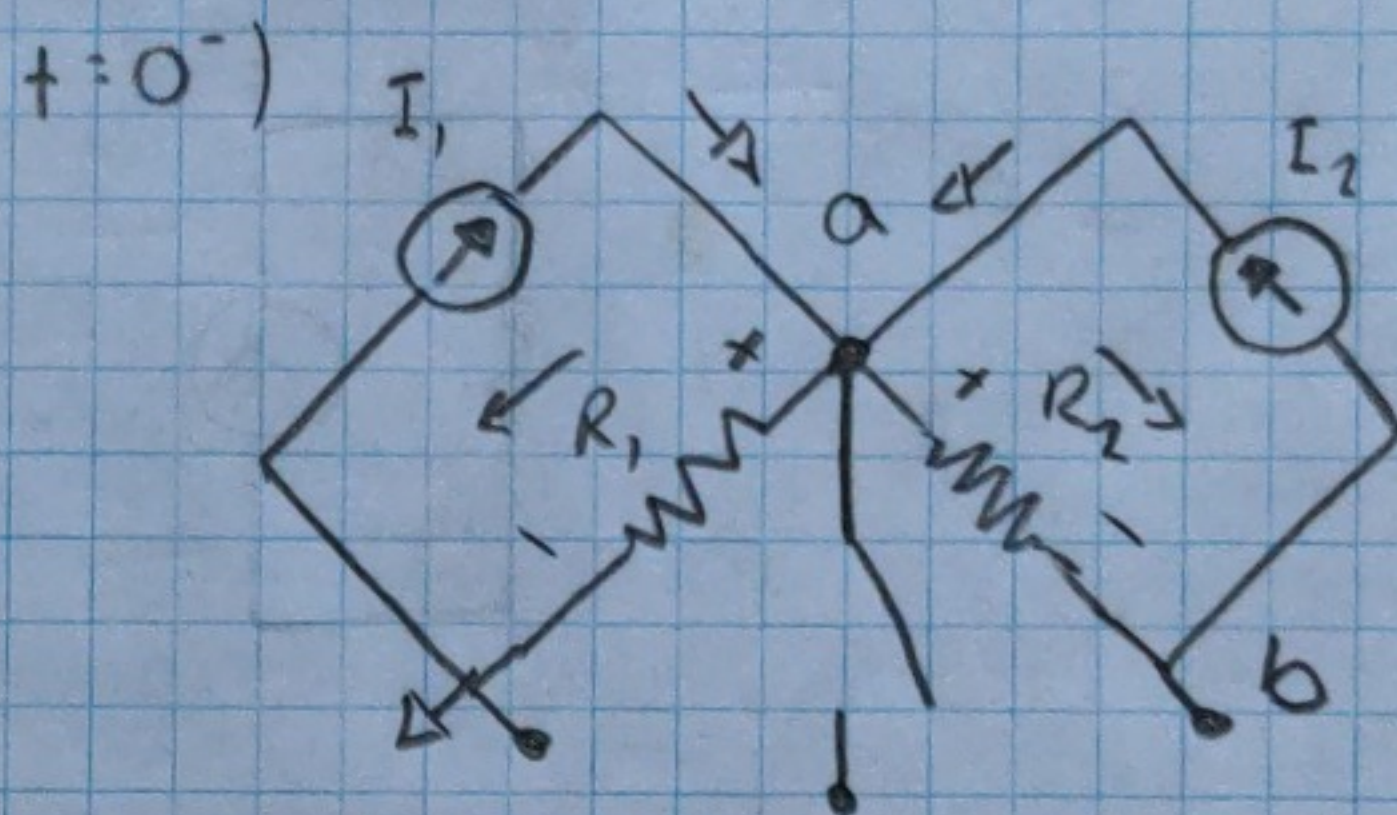

KCL @ a) $I_1 + I_2 = i_{R_1} + i_{R_2}$
 $4A + 2A = i_{R_1} + i_{R_2}$

i_{R_2} must equal I_2 and i_{R_1} must equal I_1

$$V_a = I_1 \cdot R_1 = 4A \cdot 1\Omega = 4V$$

$$V_{R_2} = I_2 \cdot R_2 = 12V$$

$$V_b = V_a - V_{R_2} = 4V - 12V = \boxed{-8V = V_C}$$




5.3) cont.

$$t = 0^+ \quad \frac{dV_C}{dt} = \frac{i_C}{C}$$

Since there is no current through the inductor at $t = 0^+$ there is no current through the capacitor
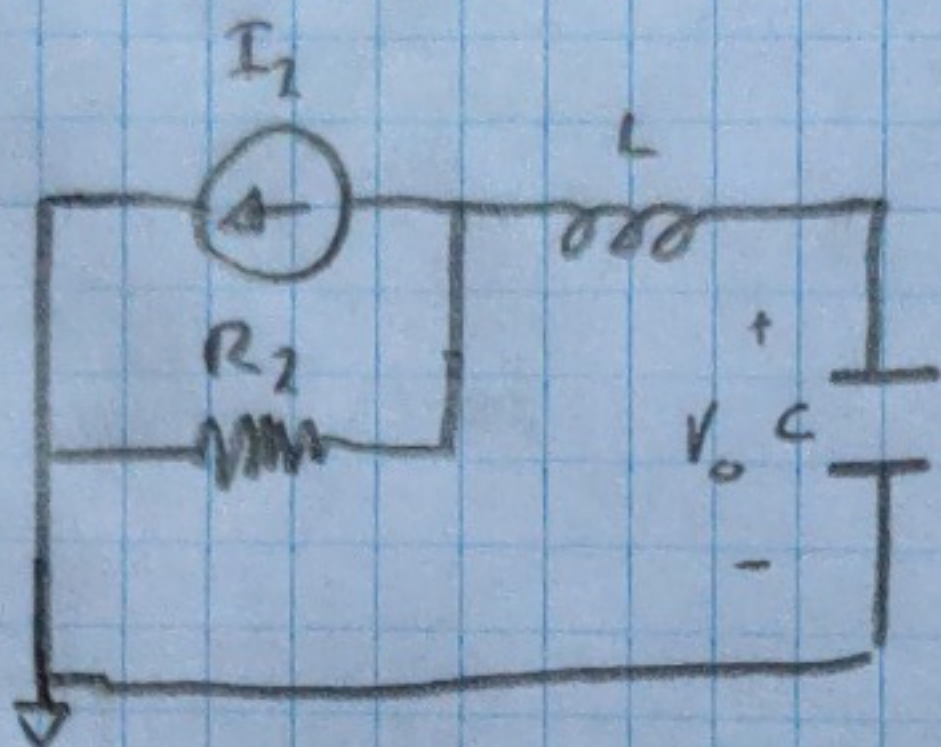
$$\frac{dV_C}{dt} = \frac{0A}{40mF} = 0V/s$$



$$\alpha = \frac{6\pi}{2(1H)} = 3 \text{ NP/s}$$

$$\omega_0 = \frac{1}{\sqrt{1H \cdot 40mF}} = 5 \text{ rad/s}$$

$\alpha < \omega_0$ underdamped

$$\omega_d = \sqrt{25 - 9} = 4 \text{ rad/s}$$

$$v(t) = e^{-3t} (B_1 \cos(4t) + B_2 \sin(4t))$$

$$\frac{dv(t)}{dt} = -3e^{-3t} (B_1 \cos(4t) + B_2 \sin(4t)) + e^{-3t} (-4B_1 \sin(4t) + 4B_2 \cos(4t))$$

$$v(0^+) = -8V = e^0 (B_1 \cos(0) + B_2 \sin(0))$$

$$-8V = B_1$$

$$\frac{dv(0^+)}{dt} = 0V/s = -3B_1 + 4B_2$$


$$0V/s = 24 + 4B_2$$

$$-24 = 4B_2$$

$$B_2 = -6V$$

$$v(t) = e^{-3t} (-8 \cos(4t) - 6 \sin(4t)) V$$

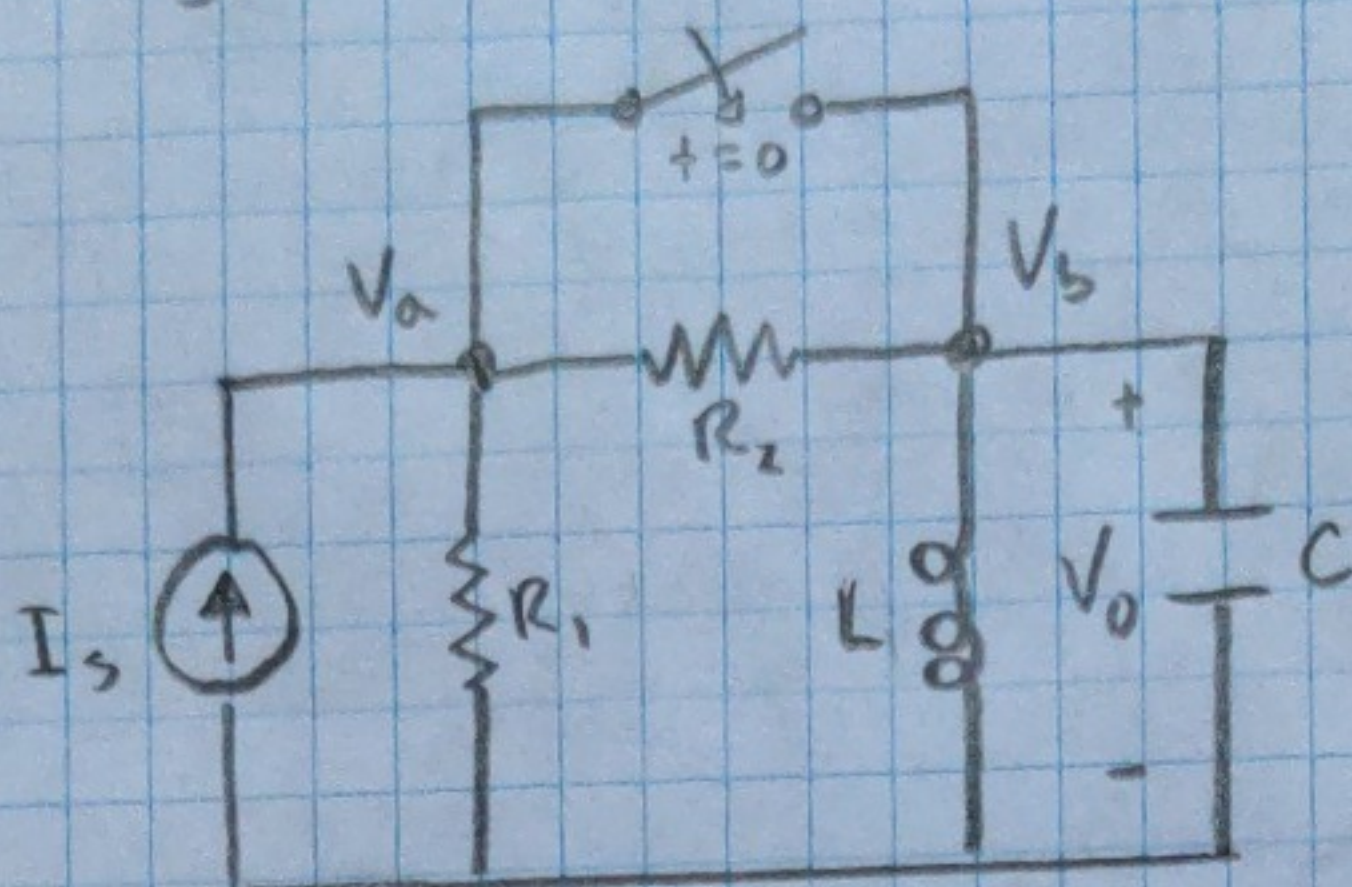5.4) Find the output voltage $V_o(t)$. The switch has been open for a long time and closes at $t=0$



$$I_s = 3A \quad R_1 = 5\Omega$$

$$R_2 = 10\Omega \quad L = 1H$$

$$C = 10mF$$

At $t=0^-$ L acts as a short circuit to ground. Therefore $V_b(0^-) = 0V = V_o(0^-)$.

The current through L will be the same as the current through R_1 .

$$i_L(0) = I_s \left(\frac{R_1}{R_1 + R_2} \right) = 3A \left(\frac{5\Omega}{15\Omega} \right) = 1A$$

t	i_L	V_c	$\frac{dV_c}{dt}$	$\frac{di_L}{dt}$
0^-	1A	0V	200V/s	0A/s
0^+	1A	0V	200V/s	0A/s
∞	3A	0V	200V/s	0A/s

At $t=0^+$ Since the capacitor maintains the voltage at V_b and now $V_a = V_b$ there is no current across R_1 or R_2 .

Find i_c) $I_s = i_L + i_c$

$$3A = 1A + i_c \rightarrow i_c = 2A$$

$$\frac{dV_c}{dt} = \frac{2A}{10mF} = 200V/s$$


$$\frac{di_L}{dt} = \frac{0V}{1H} = 0A/s$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(5\Omega)(10mF)} = 10^4/s \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10^4 rad/s$$

$\alpha = \omega_0 \rightarrow$ critically damped.

$$V(t) = (A_1 + A_2 t) e^{-\alpha t}$$
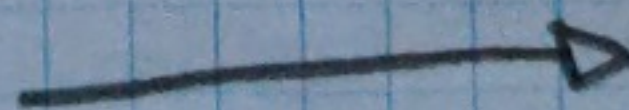
$$\frac{dV(t)}{dt} = A_2 e^{-\alpha t} + (A_1 + A_2 t) (-\alpha) e^{-\alpha t}$$



Chris Hunt

HW5

ENGR 203

S.4) cont.

$$V(0) = 0 \text{ V} = A_1$$

$$\frac{dV(0)}{dt} = 200 \text{ V/s} = A_2 e^0 - 10A_1$$

$$200 \text{ V/s} = -10A_1 \rightarrow A_1 = -20 \text{ A}$$

$$V_0(t) = -20te^{-10t} \text{ V}$$