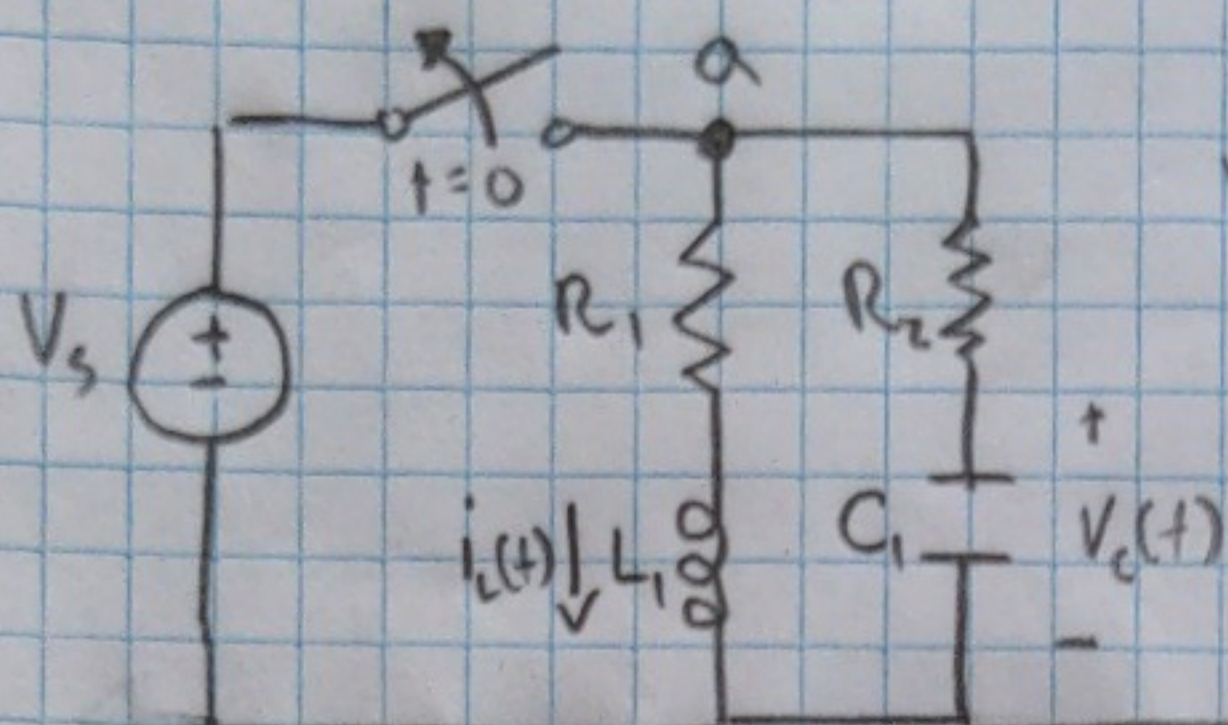


4.1) The switch has been closed for a long time, at $t=0$ the switch opens.

Find: a) $i_L(0^+)$, $V_C(0^+)$ b) $\frac{di_L(0^+)}{dt}$, $\frac{dV_C(0^+)}{dt}$ c) $i_L(\infty)$, $V_C(\infty)$



$$V_s = 12V$$

$$R_1 = 6\Omega \quad R_2 = 4\Omega$$


$$C = 400mF \quad L = 2H$$

At $t=0^-$ the voltage across the capacitor will equal V_a and will have 0 current. While the current across the inductor will be the current through the branch, V_a/R_1 .

Answers:

t	$i_L(t)$	$V_C(t)$	$\frac{di_L}{dt}$	$\frac{dV_C}{dt}$
0^-	2A	12V		
0^+	2A	12V	-4A/s	5V/s
∞	0A	0V		

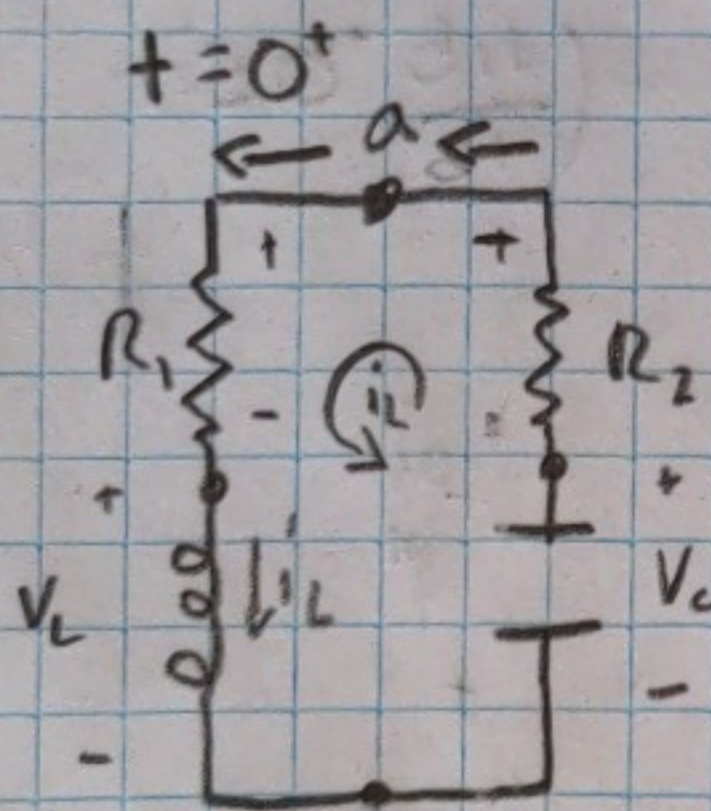At $t=0^+$ since the capacitor cannot tolerate discontinuous voltages V_C will equal 12V. Likewise, the current across an inductor cannot change instantaneously, i_L will equal 2A.



KCL @ a) $i_C = i_L = 2A$

KVL) $+V_L + (-V_C) + V_{R_2} + V_{R_1} = 0$

$$+V_L - 12V + (2A \cdot 4\Omega) + (2A \cdot 6\Omega) = 0$$

$$V_L = -8V$$

Find $\frac{di_L}{dt}$


$$\frac{di_L}{dt} = \frac{V_L(0^+)}{L} = \frac{-8V}{2H} = -4A/s$$

Find $\frac{dV_C}{dt}$

$$\frac{dV_C}{dt} = \frac{i_C(0^+)}{C} = \frac{2A}{400mF} = 5V/s$$

4.2) For the following circuit, Find:

t	i_L	V_C	V_R	$\frac{di_L}{dt}$	$\frac{dV_C}{dt}$	$\frac{dV_R}{dt}$
0^-	0A	-10V	0V	0A/s	0V/s	0V/s
0^+	0A	-10V	0V	0A/s	8V/s	0V/s
∞	0.4A	6V	16V	0A/s	0V/s	0V/s

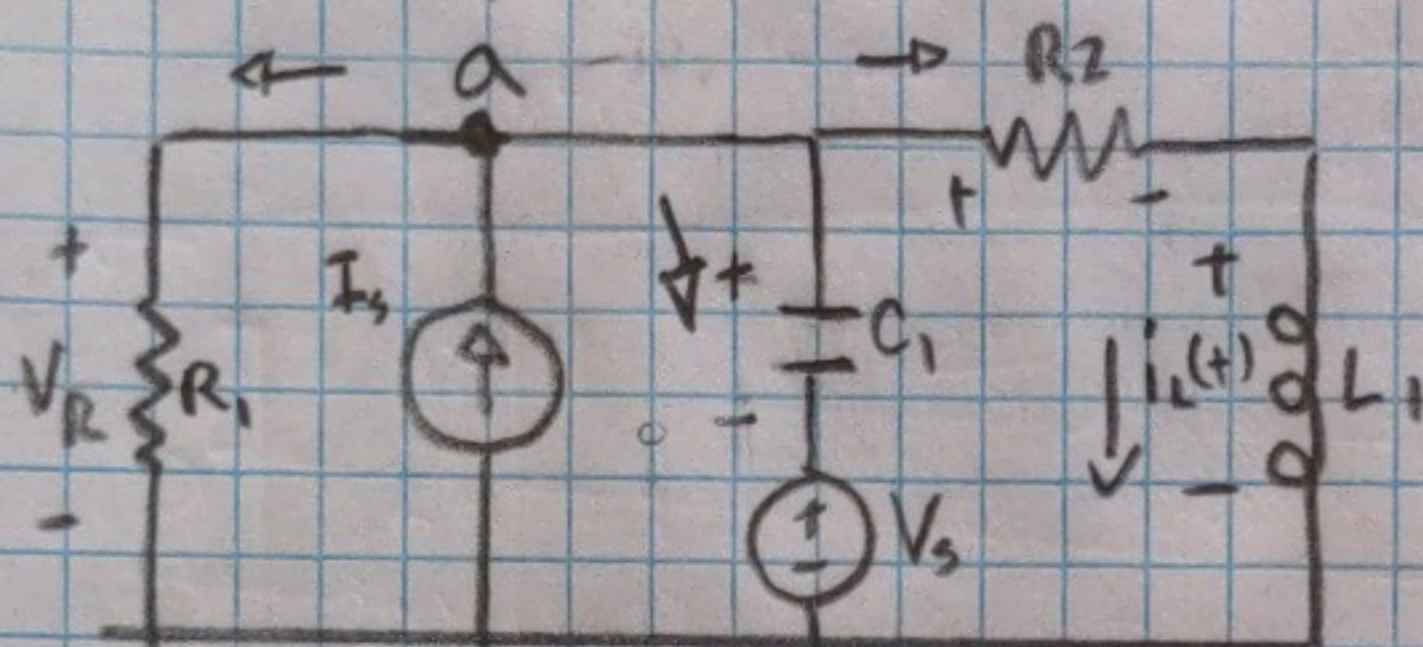

$$V_s = 10V \quad I_s = 2u(t)A$$

$$R_1 = 10\Omega \quad R_2 = 40\Omega$$

$$C_1 = 250mF \quad L_1 = 125mH$$

At $t=0^-$ the capacitor acts as an open circuit, so there is a voltage across C_1 , but no current able to flow through any circuit branches, and no voltage difference across R_1 .

At $t=0^+$ since the capacitor cannot tolerate instantaneous voltage changes $V_C(0^+) = V_C(0^-)$ and since inductors cannot tolerate instantaneous changes in current $i_L(0^+) = i_L(0^-) = 0A$. Since there is no voltage change at node 'a' the voltage across R_1 stays the same, 0V.

Find $\frac{dV_C}{dt}$ (KCL) $I_s = i_{R_1} + i_C + i_L$

$$2A = 0 + i_C + 0$$

$$i_C = 2A$$

$$\frac{dV_C(0^+)}{dt} = \frac{2A}{250mF} = 8V/s$$


Find $\frac{di_L}{dt}$ (KVL) $-V_s - V_C + V_{R_2} + V_L = 0$

$$-10V - (-10V) + V_{R_2} + V_L = 0$$

$$V_L = 0V \rightarrow \frac{di_L(0^+)}{dt} = \frac{0V}{125mH} = 0A/s$$

Find $\frac{dV_R}{dt}$ $\frac{dV_R}{dt} = \frac{d(i_{R_1} R_1)}{dt} = 0V/s$

4.2) Cont.

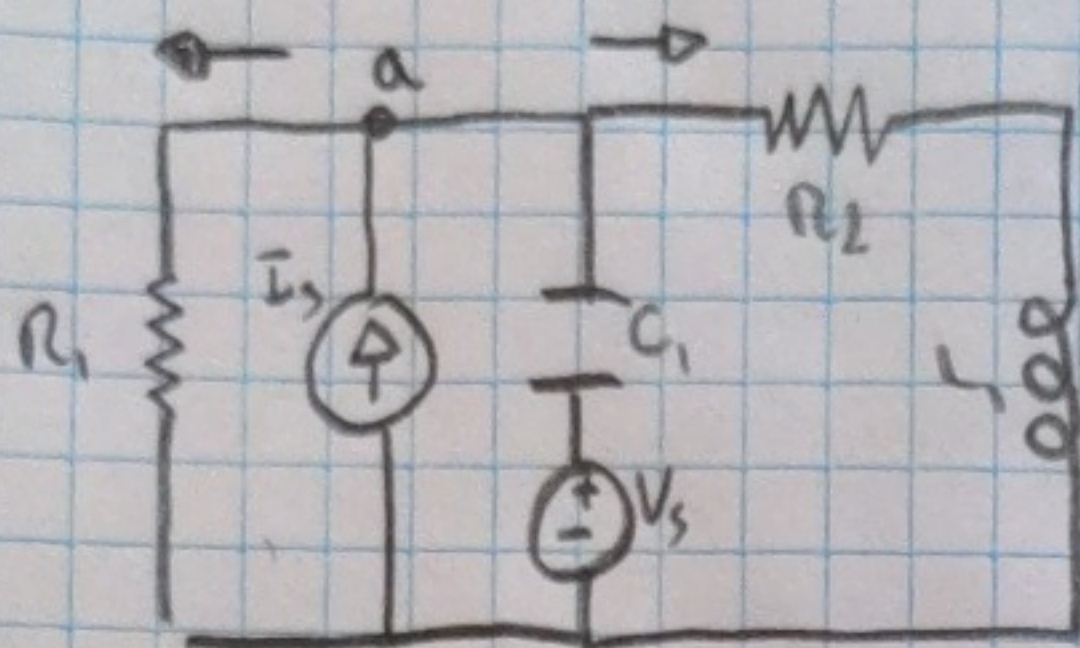At $t = \infty$ Find $i_{R_1}(\infty)$ and $i_L(\infty)$

Use a current divider.

$$i_L = 2A \left(\frac{10\Omega}{50\Omega} \right) = 0.4A$$


$$i_{R_1} = 2A - 0.4A = 1.6A$$

Find $V_R(\infty)$ $V_R(\infty) = i_{R_1} \cdot R_1 = 1.6A \cdot 10\Omega = 16V$

Find $V_C(\infty)$ $V_C(\infty) = V_R(\infty) - V_s = 16V - 10V = 6V$

4.3) For the following circuit, Find:

t	i_L	V_C	i_{R_1}	V_{R_2}	$\frac{di_{R_1}}{dt}$	$\frac{dV_{R_2}}{dt}$	$\frac{dV_C}{dt}$
0^-	$0A$	$0V$	$0A$	$0V$	0A/s	0V/s	0V/s
0^+	$0A$	$0V$	$0A$	$0V$	$0A/s$	$0V/s$	$16V/s$
∞	$1.6A$	$9.6V$	$2.4A$	$9.6V$	0A/s	0V/s	0V/s

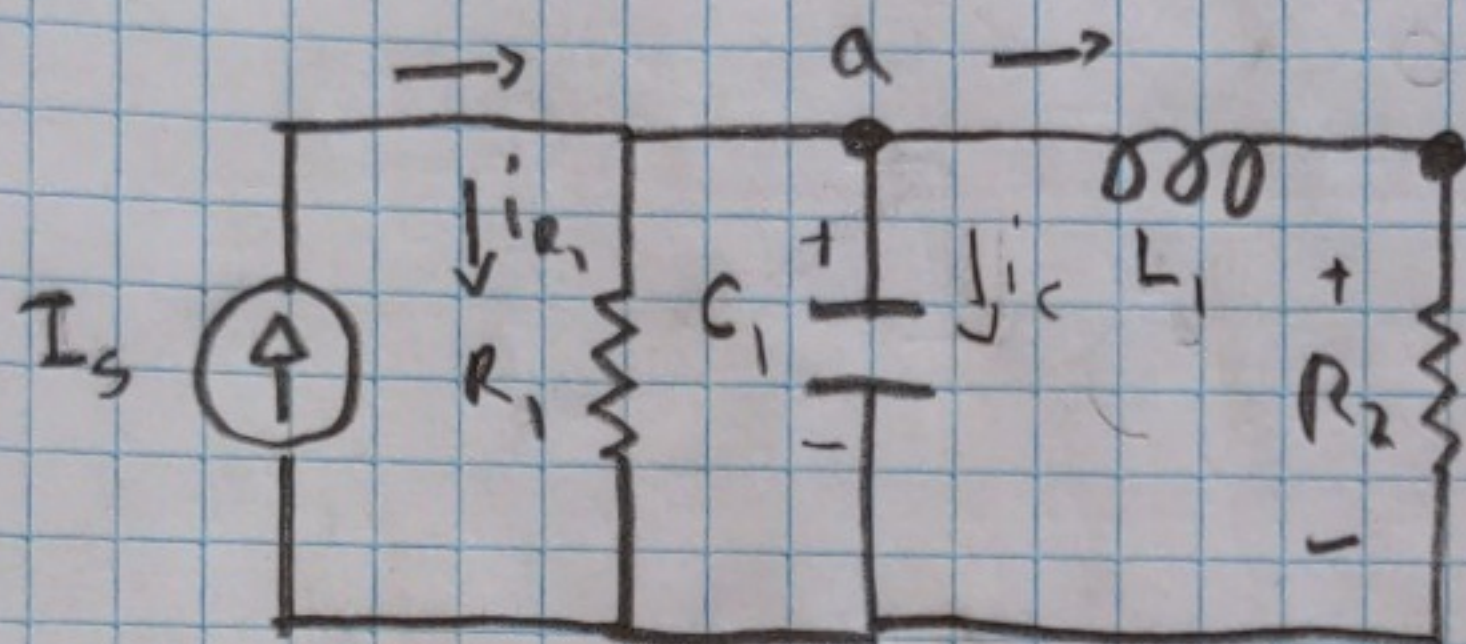

$$I_s = 4u(t) A$$

$$R_1 = 4\Omega \quad R_2 = 6\Omega$$

$$C_1 = 250mF \quad L_1 = 1H$$

At $t=0^-$ there is no source current or voltage. All values are zero

At $t=\infty$ the capacitor acts as an open circuit and the inductor acts as a short circuit.

Find $i_{R_1}(\infty)$ $i_{R_1}(\infty) = 4A \left(\frac{6\Omega}{10\Omega} \right) = 2.4A$

Find $V_{R_2}(\infty)$ $V_{R_2}(\infty) = V_a(\infty) = 2.4A \cdot 4\Omega = 9.6V$

At $t=0^+$ however, the current source initiates 4A of current, changing the circuit dynamics. The capacitor maintains the voltage of 0V at node a and the inductor maintains 0A of current down its branch. With no voltage across R_1 there is no current

Find $\frac{dV_C(0^+)}{dt}$ KCL @ a) $I_s = i_{R_1} + i_L + i_C$

$$4A = 0 + 0 + i_C$$

$$i_C(0^+) = 4A \rightarrow$$

$$\frac{dV_C(0^+)}{dt} = \frac{4A}{250mF} = 16V/s$$

Chris Hunt

HW4

ENGR 203

4.3) cont.

Find $\frac{di_L}{dt}$) KVL) $-V_C + V_L + V_{R_2} = 0$

$$0 + V_L + i_L(0^+) \cdot 6\Omega = 0$$

$$V_L = 0 \rightarrow \frac{di_L(0^+)}{dt} = \frac{0V}{1H} = 0 A/s$$

Find $\frac{dV_R}{dt}$)

$$\frac{dV_{R_2}(0^+)}{dt} = \frac{d}{dt}(i_L R_2) = 0 V/s$$

4.4) The current in an RLC series circuit is described by:

$$\frac{d^2 i}{dt^2} + 10 \frac{di}{dt} + 25i = 0 \quad i(0) = 10A \quad \frac{di(0)}{dt} = 0A/s$$

Find $i(t)$ For $t > 0$:

$$\frac{R}{L} = 10 \quad \frac{1}{LC} = 25$$

$$\alpha = \frac{R}{2L} = \frac{1}{2} \cdot 10 = 5 \text{ NP/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \left(\frac{1}{LC}\right)^{.5} = (25)^{.5} = 5 \text{ rad/s}$$

$\alpha = \omega_0$
Critically damped

$i(t)$ For the critically damped circuit $i(t) = (A_2 + A_1 t) e^{-\alpha t}$

$$i(t) = (A_2 + A_1 t) e^{-5t}$$

Find $\frac{di(t)}{dt}$ $\frac{di(t)}{dt} = A_1 e^{-5t} - 5(A_2 + A_1 t) e^{-5t}$

$$i(0) = 10A = A_2$$

$$\frac{di(0)}{dt} = 0A/s = A_1 - 5A_2$$

$$A_2 = 10A \rightarrow 0A/s = A_1 - 5(10) \rightarrow A_1 = 50$$

Therefore, $i(t) = (10 + 50t) e^{-5t}$